

*We strongly recommend that you read about a topic before it is covered in lectures.*

| Lecture Date | Topics Covered   | Reading from Giancoli  |
|--------------|--|--|
| #9 Mon 2/25  | Currents - Resistivity - Ohm's Law   | Chapter 25 through Sect. 25-4  |
| #10 Wed 2/27 | Batteries - EMF - Energy Conservation - Power<br>Kirchhoff's Rules - Circuits<br><i>Kelvin Water Dropper</i> | Sect. 25-5 through 25-8<br>Chapter 26 through Sect. 26-3<br><i>(take notes in lecture)</i> |
| #11 Fri 3/1  | Magnetic field - Lorentz force - Torques<br>Electric Motors (DC)<br>Cathode Ray Tube, Oscilloscope           | Chapter 27 through Sect. 27-7<br>Sect. 23-9  |

**Due before 4 PM Friday, March 1 in 4-339B.**


**Problem 3.1**

*Capacitors in series and parallel.*  
Giancoli 24-23.

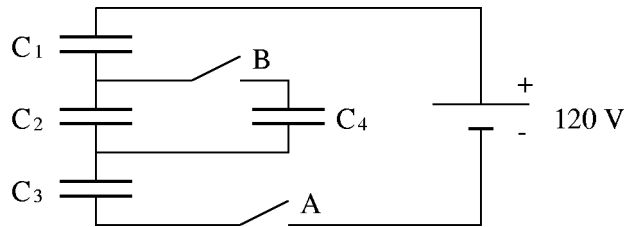**Problem 3.2**

*Switching Capacitors.*

In the diagram below, the four capacitors have the same capacitance; the battery provides 120 V.



Consider two cases, starting in both cases with uncharged capacitors.

**Case I.**

- (a) While switch B is kept open, switch A is closed and then opened after  $C_1$ ,  $C_2$ , and  $C_3$  are fully charged. What is now the electric potential difference across each capacitor?
- (b) Subsequently switch B is closed. What is now the electric potential difference across each capacitor?

**Case II.**

- (c) Switch A is open. Switch B is first closed. What is now the electric potential difference across each capacitor?
- (d) Subsequently switch A is closed. What now is the potential difference across each capacitor?

**Problem 3.3.**

*The effect of a dielectric medium on the capacitance.*  
Giancoli 24-60.

**Problem 3.4***Comparing cylindrical and spherical capacitors.*

- (a) Compare the capacitance of a capacitor of 2 concentric spheres with  $R_1 = 6$  cm and  $R_2 = 9$  cm, with that of a cylindrical capacitor having the same radii and axial length of 15 cm. Why are the capacitance values nearly equal?
- (b) Show that, when  $R_1$  and  $R_2$  are nearly equal ( $R_2 = R_1 + \delta$ ;  $\delta \ll R_1$ ) the formulas for the spherical and cylindrical capacitors may be approximated by the formula for the parallel-plate capacitor,  $C = \epsilon_0 A/d$  (eq. 24-2). *Hint: make use of Taylor's expansion in terms of  $\delta/R_1$ .*

**Problem 3.5***The Van de Graaff*

The spherical dome of a Van de Graaff electrostatic generator has a radius of  $R$  m. A rubberized belt 50 cm wide travels at a velocity of 30 m/sec. The belt is given a surface charge density which produces a field of approximately  $10^6$  V/m on each side of the belt. (see Figure 23-37 on page 612).


- (a) What is the current carried by the belt?
- (b) What is the maximum charge that the spherical dome can hold, and how long will it take to reach this value?
- (c) What is the maximum electrostatic potential of the spherical dome?
- (d) What are your answers under (b) and (c) for  $R = 0.15$  and  $R = 0.5$  m?

**Problem 3.6***Resistor Circuit.*

Giancoli 26-25

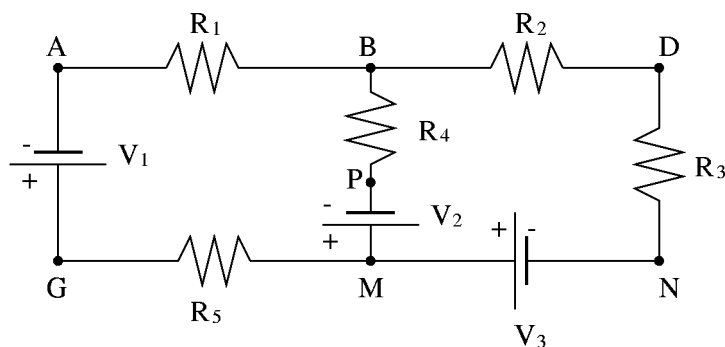**Problem 3.7***Resistor Network.*

A circuit consists of 5 resistors and 3 batteries (see diagram); the connecting wires have all a negligible resistance. The values for  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ , and  $R_5$  are  $10\ \Omega$ ,  $30\ \Omega$ ,  $50\ \Omega$ ,  $70\ \Omega$ , and  $100\ \Omega$ , respectively. The batteries have a negligible internal resistance; their voltages  $V_1$ ,  $V_2$ , and  $V_3$ , are 12 V, 24 V, and 36 V, respectively (for their polarities, see the diagram).



- (a) Calculate the current (magnitude and direction) of the currents through each of the 5 resistors.
- (b) What is the potential difference (observe signs!) between the points A&P, P&N, and G&D.

**Problem 3.8***Wire resistance.*

Giancoli 25-52.

**Problem 3.9**

*Energy consumption of heater.*

Giancoli 25-61.

**Problem 3.10**

*Electric car.*

Giancoli 25-72.

**Recitations.**

There are 28 recitation sections (see the 8.02 Website). If *for any reason* you want to change section, please see Maria Springer in 4-352.